


EDWARD ESKAY
DEPARTMENT OF PHYSICS
OLABISI ONABANJO UNIVERSITY, AGO - IWOYE
2017/2018 RAIN SEMESTER EXAMINATION

Time: 1hr, 30mins


PHY 202: ELECTRIC CIRCUITS AND ELECTRONICS

Instruction: Answer any three (3) questions

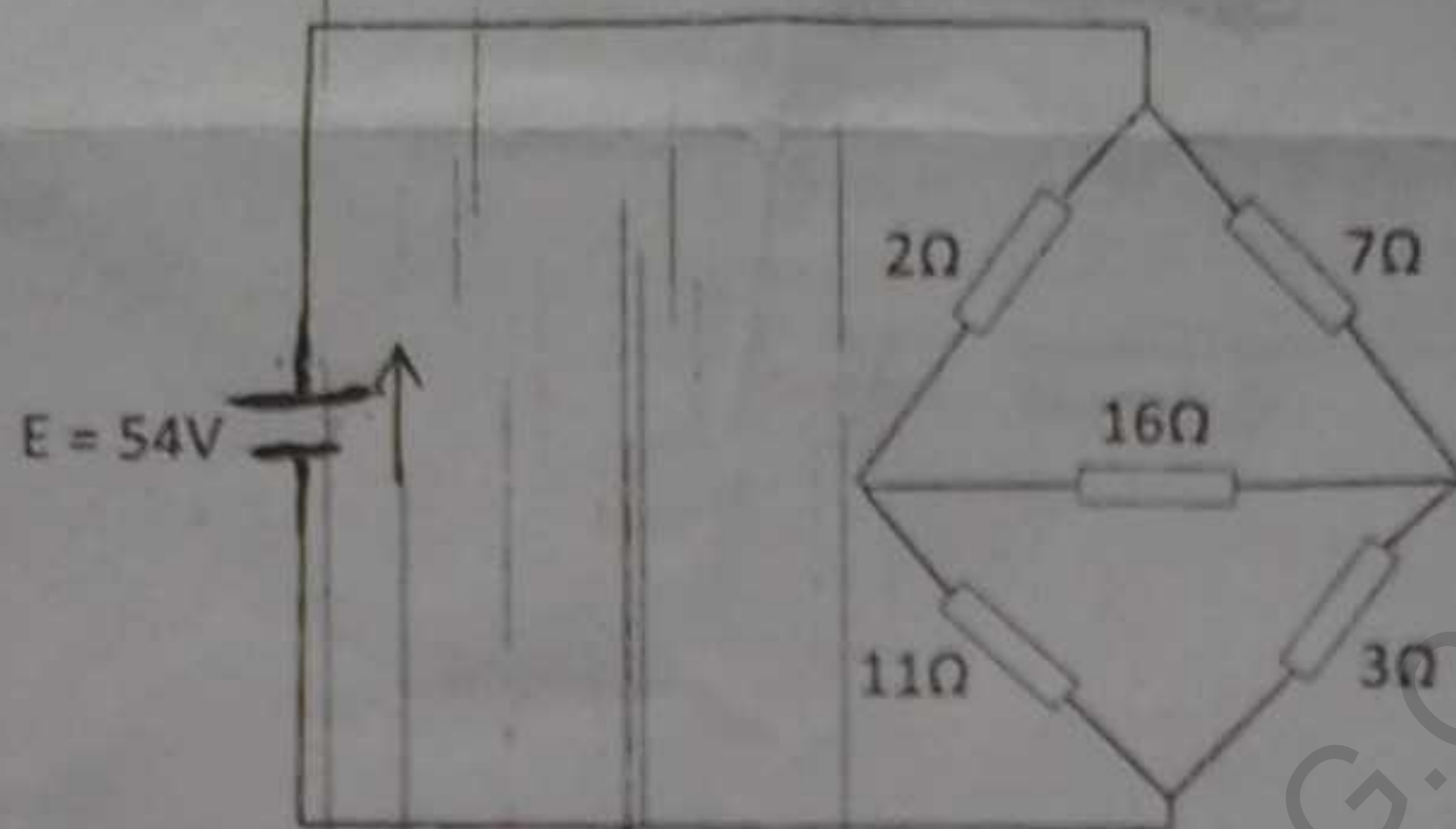- 1a State Kirchhoff's laws ✓
b Using Thevenin's theorem, calculate the current flowing through the 16Ω - resistor of the Wheatstone bridge network shown in the diagram below.




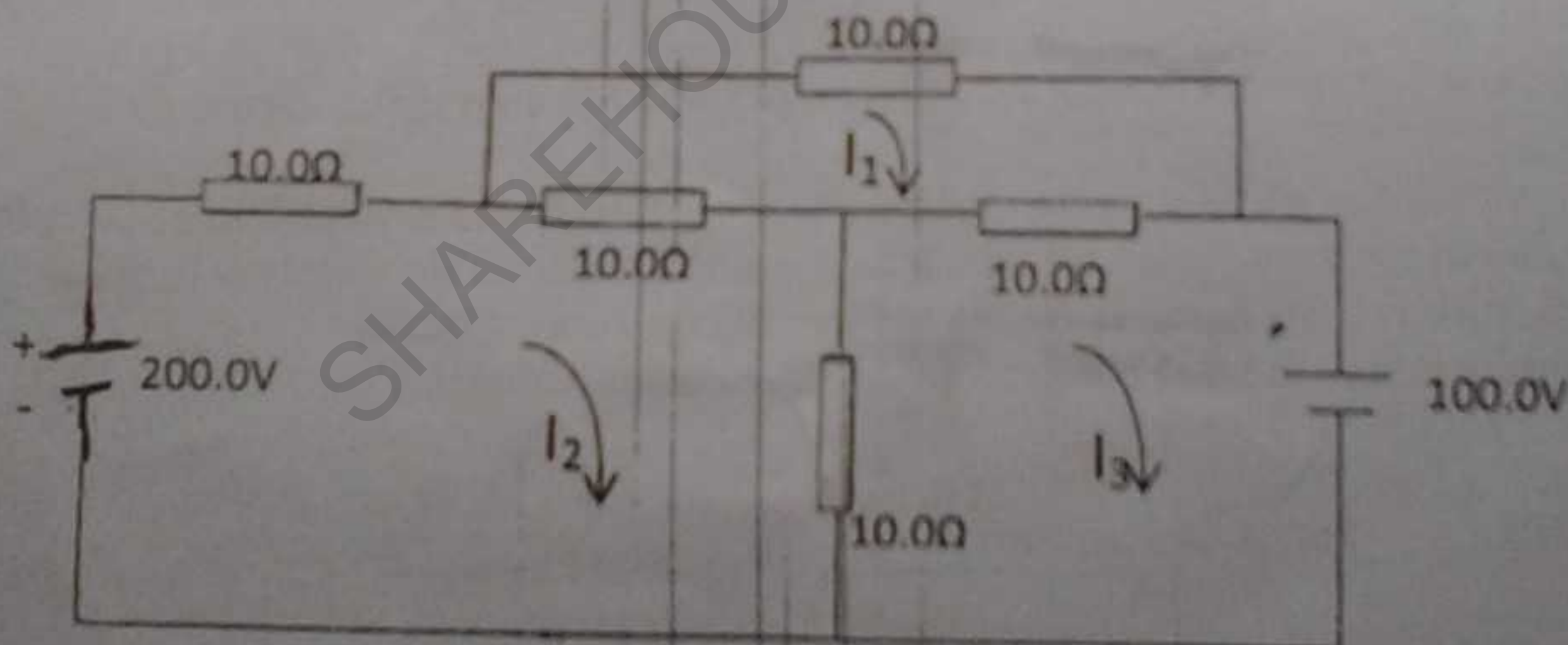- c (i) Find the intrinsic carrier concentration in Silicon at 300°K for which $N = 3 \times 10^{25} \text{ m}^{-3}$, $E_g = 1.1 \text{ eV}$, $\mu_e = 0.14 \text{ m}^2/\text{VS}$ and $\mu_h = 0.05 \text{ m}^2/\text{VS}$.
(ii) Find the conductivity of the silicon
- 2a State Thevenin's theorem; and highlight the procedures of thevenizing a circuit.



- (2b) Obtain the values for the currents I_1 , I_2 and I_3 in given circuit above using Resistance Matrix Method.
(2c) A bipolar transistor has a common-emitter current gain of 125. If the transistor operates with a collector current of 50 mA , determine the value of base current.

- 3a Define the following
- Intrinsic Semiconductor
 - Doping
 - Barrier Voltage
 - Depletion Layer
 - Biasing
- b A voltage source delivers 4A when the load connected to it is 5Ω and 2A when the load becomes 20Ω . Calculate
- maximum power which the source can supply
 - power transfer efficiency of the source with R_L of 20Ω
 - the power transfer efficiency when the source delivers 60W.
- 4a A coil with a resistance of 5Ω and an inductance of $0.02H$ is arranged in parallel with another coil having a resistance of 1Ω and an inductance of $0.08H$. Calculate the current through the combination and the power absorbed when a voltage of 100V at 50Hz is applied. Estimate the resistance of a single coil which will take the same current at the same power factor.

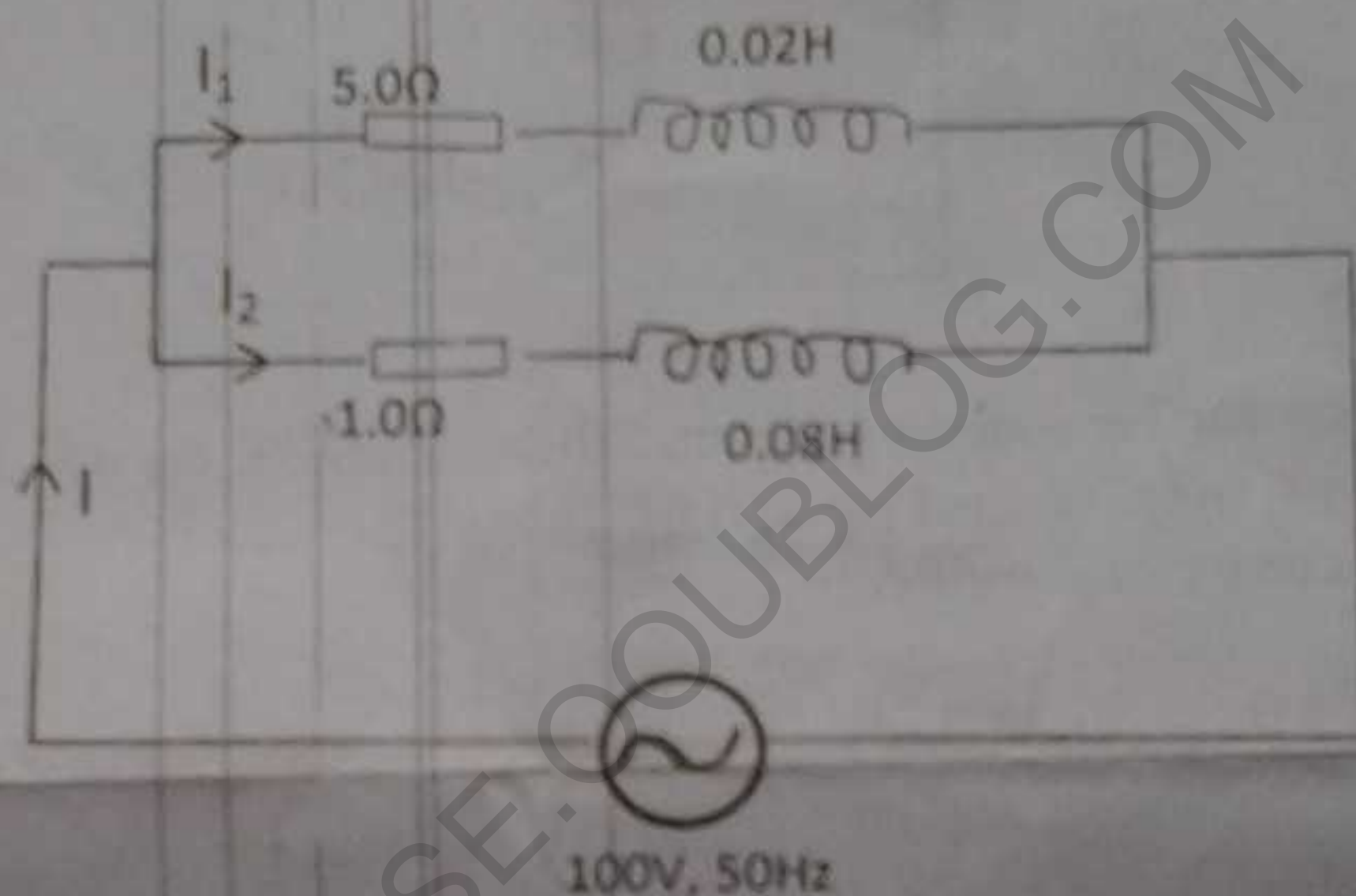

- 4b Briefly explain how N-type semiconductor can be obtained from a given element.
- 5a A capacitor is connected in parallel with a coil having $L = 5.52mH$ and $R = 10\Omega$ to a 100V, 50 Hz supply. Calculate the value of the capacitance for which the current taken from the supply is in phase with voltage.
- 5b In a tabular form, differentiate between Series and Parallel Resonant Circuits.
- 5c Calculate the current across the 4Ω resistor in the figure below using any method of your choice.

